



GARISSA UNIVERSITY

UNIVERSITY EXAMINATION **2017/2018** ACADEMIC YEAR **ONE**
SECOND SEMESTER EXAMINATION

SCHOOL OF EDUCATION, ARTS AND SOCIAL SCIENCES

FOR THE DEGREE OF BACHELOR OF EDUCATION (ARTS)

COURSE CODE: COM212

COURSE TITLE:

EXAMINATION DURATION: 3 HOURS

DATE: /12/17

TIME: .00-.00 PM

INSTRUCTION TO CANDIDATES

- The examination has SIX (6) questions
- Question ONE (1) is COMPULSORY
- Choose any other THREE (3) questions from the remaining FIVE (5) questions
- Use sketch diagrams to illustrate your answer whenever necessary
- Do not carry mobile phones or any other written materials in examination room
- Do not write on this paper


This paper consists of TWO (2) printed pages

please turn over



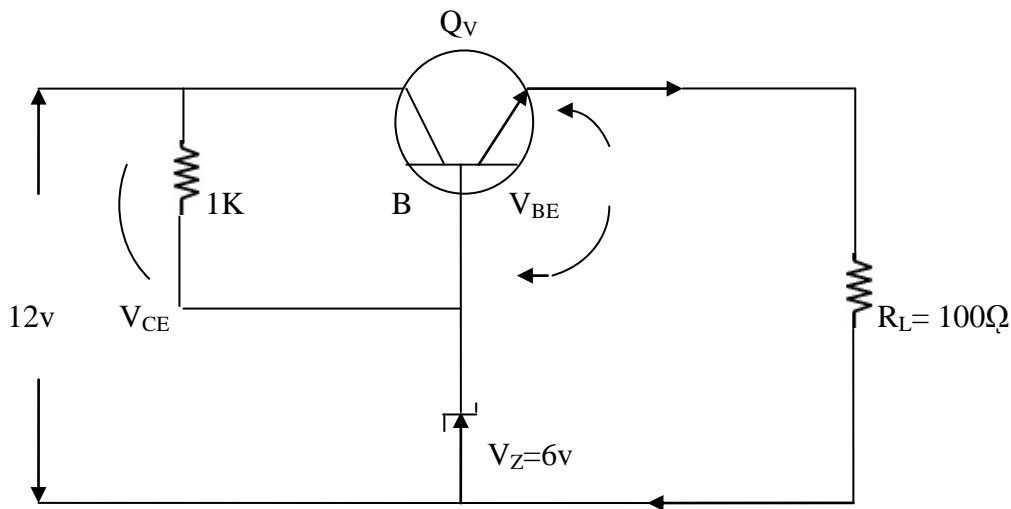QUESTION ONE (COMPULSORY)

- (a). i. Determine the valency electrons of Gallium with an atomic number of 31. [2 marks]
 - ii. Atomic nuclei are made of protons and neutrons. This fact by itself shows that there must be another kind of interaction in addition to the electrical forces. Explain [2 marks]
 - iii. With reference to energy bands explain electrical conduction and atomic structure of Conductors, Insulators and Semiconductors. [6 marks]
- (b). Using the emitter follower regulation circuit below compute the values of




- i. V_L [2 marks]
 - ii. I_E [2 marks]
 - iii. Power dissipated by Q_v [3 marks]
- (d). i. Identify advantages of digital signals over analog signals. [3 marks]
- ii. Comment on the electrical conductivity of metals and semiconductors. [2 marks]
 - iii. Explain the purpose of electronic voltage regulators in computers, automobile alternators and central power station. [3 marks]

QUESTION TWO (15 MARKS)

- (a). State three regions in which a BJT transistor operates. [3 marks]
- (b). i. Explain why the collector region of most transistors are larger than Emitter and Base regions. [2 marks]
- ii. With the aid of illustrations discuss pnp transistor biasing of emitter-base junction.



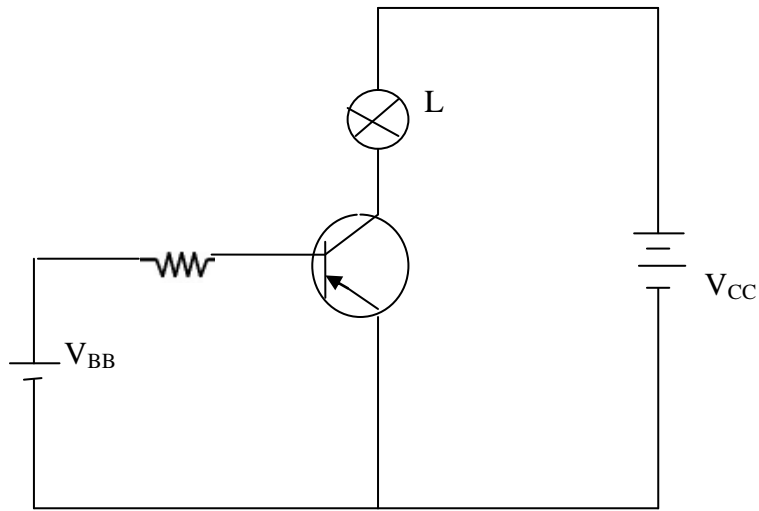- iii. The figure below shows a lamp in a transistor circuit configuration. State and explain if the lamp is ON or OFF. [4 marks]




- iv. Define common emitter forward amplification factor β_{dc} . [2 marks]

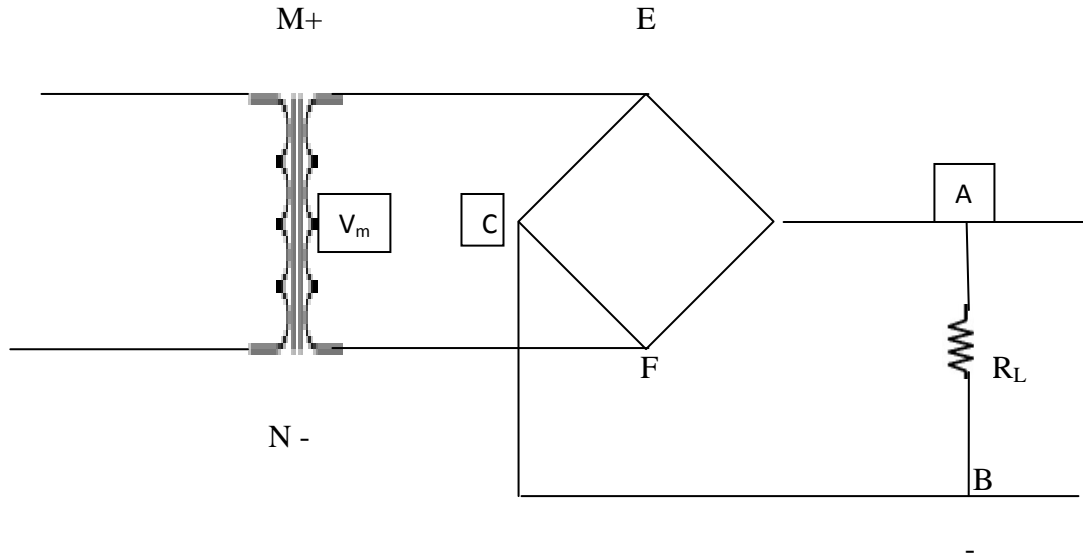QUESTION THREE (15 MARKS)

- (a). i. State function of a voltage regulator . [2 marks]
- ii. Regulated power supply systems include transformers, rectifiers and regulators. Outline the functions of the above named power blocks showing input/output relation. [5 marks]
- (b). Define rectification. [1 mark]
- (c). The circuit below shows full wave bridge rectifier circuit.






- i. Complete the circuit and show current direction through the load resistor R_L [2 marks]
- ii. Explain using illustrations full wave rectification in c(i) above [5 marks]

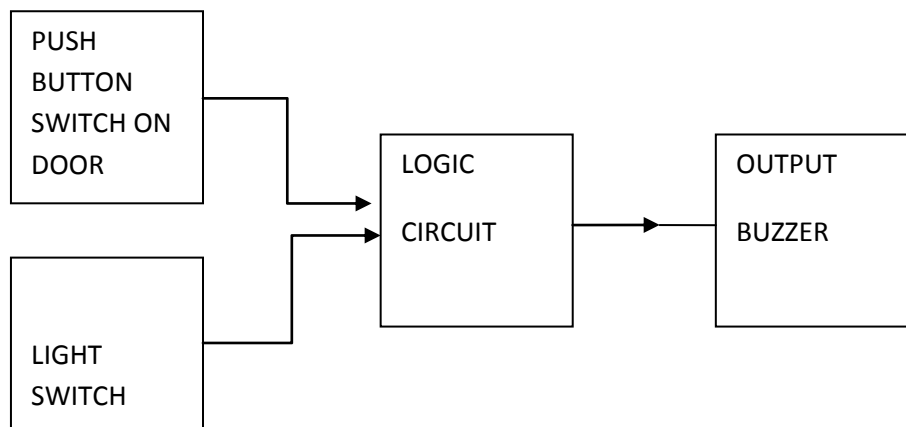QUESTION FOUR (15 MARKS)

- (a). Define logic gate. [1 mark]
- (b). i. The following operations represent common gates. Identify their symbols [3 marks]
 - AND:
 - OR:
 - NOT:
- ii. Most new cars have audible alarm systems. The block diagram of lights –on alarm system is as shown below



The table below shows combinations of switches for the lights-on-alarm.

| Light switch | Door switch | Audible warning |
|--------------|-------------|-----------------|
| OFF | OPEN | OFF |
| OFF | CLOSED | OFF |
| ON | OPEN | OFF |
| ON | CLOSED | ON |

By choosing the correct logic gate design a system using a truth table which could be used to make the decisions necessary in the lights-on warning system in a car. [5 marks]

- (c). i. State two advantages of a bridge rectifier. [2 marks]
- ii. Discuss biasing of a p-n junction diode. [4 marks]

QUESTION FIVE (15 MARKS)


- (a). i. Define an integrated circuit (IC). [1 mark]
- ii. Outline three applications of IC's in modern electronic market. [3 marks]
- iii. Distinguish between monolithic and multichip IC's. [2 marks]
- (b). i. What do you understand by the terms computer hardware and software. [2 marks]
- ii. Can a computer run without a software or hardware? Discuss [2 marks]
- iii. Illustrate ways of installing a computer hardware with reference to computer processor and hard drive. [5 marks]




QUESTION SIX (15 MARKS)

(a). i. State the functions of a flip flop. [2 mark]

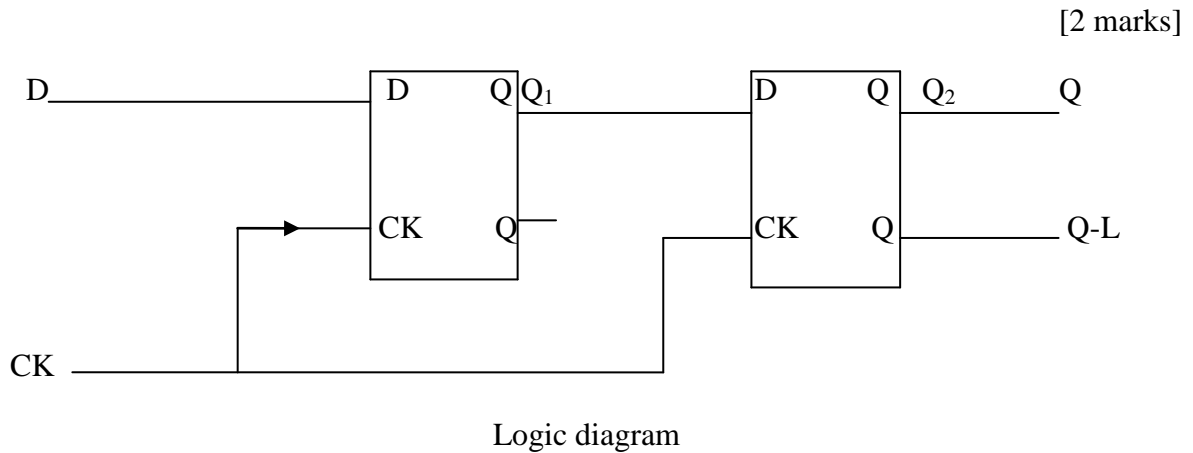ii. The figure below shows a positive-edge triggered flip flop. Discuss its function. [2 marks]



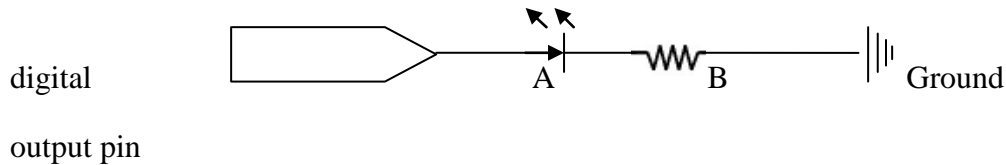iii. The electronic diagram below shows a circuit of a microcontroller. Name the parts labeled A and B [2 marks]



iv. Discuss how the parts in a(iii) above are connected to a breadboard and wiring board using jumper cables. [3 marks]

(b). Surveying the rules for Boolean addition, the 0 and 1 values seem to resemble the truth table of a very common logic gate. Which type of gate is this, and what does this suggest about the relationship between Boolean addition and logic circuits? [6 marks]

Rules for Boolean addition:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$



