



GARISSA UNIVERSITY

UNIVERSITY EXAMINATION **2017/2018** ACADEMIC YEAR **TWO**
SECOND SEMESTER EXAMINATION

SCHOOL OF BIOLOGICAL AND PHYSICAL SCIENCE

FOR THE DEGREE OF BACHELOR OF SCIENCE

COURSE CODE: PHY 213

COURSE TITLE: ELECTRONICS 1

EXAMINATION DURATION: 3 HOURS

DATE: 17/04/18

TIME: 09.00-12.00 PM

INSTRUCTION TO CANDIDATES

- The examination has **SIX (6)** questions
- Question **ONE (1)** is **COMPULSORY**
- Choose any other **THREE (3)** questions from the remaining **FIVE (5)** questions
- Use sketch diagrams to illustrate your answer whenever necessary
- Do not carry mobile phones or any other written materials in examination room
- Do not write on this paper

This paper consists of **SEVEN (7)** printed pages

please turn over



QUESTION ONE (COMPULSORY)

a) Explain the difference between a metal and an insulator. **[2 marks]**

b) i. Define the terms **[2 marks]**

-Doping

-Hole

ii. Explain how temperature affects the electrical conductivity of intrinsic Semiconductors **[2 marks]**

c). Given that current gain $\beta = \frac{I_C}{I_B}$ and $\alpha = \frac{I_C}{I_E}$ show that $I_E = (\beta + 1)I_B$ and

$\alpha = \frac{\beta}{(\beta+1)}$ **[4 marks]**

ii. An intrinsic semiconductor current (I) flow is due to electrons and holes

$$I = I_e + I_h = enV_eA + e\rho V_hA \quad \text{Where } e = \text{electron charge}$$

n= no of electrons per unit

volume of conductor

v_e = electron drift velocity

v_h =hole drift velocity

ρ =hole density

Show that resistivity, $\rho = \frac{1}{en(\mu_e + \mu_h)}$ **[3 marks]**

iii. Mobilities of electrons and holes in a sample of intrinsic germanium at room temperature are $0.36\text{m}^2/\text{v-s}$ and $0.17\text{m}^2/\text{v-s}$ respectively. If the electron and hole densities are each equal to $2.5 \times 10^{-19}\text{m}^3$, Calculate germanium conductivity. **[3 marks]**

d). Briefly explain the behavior of PN junction in forward and reverse bias mode. **[3 marks]**

e). The base of PNP bipolar transistor is grounded. A battery is connected between the emitter and the base. Another battery is connected between the base and the collector. This is known as the base configuration.



- i. Draw the circuit indicating polarities of the batteries that would put the transistor in the forward active mode. Explain why you have chosen these polarities [4 marks]
- ii. Why is the emitter more heavily doped? [2 marks]

QUESTION TWO

- a). State and explain two uses of photo resistors [2 marks]
- b). i. In a zener diode circuit below state giving reasons if the zener diode is properly biased hence the diode current assuming it to be an ideal one [5 marks]

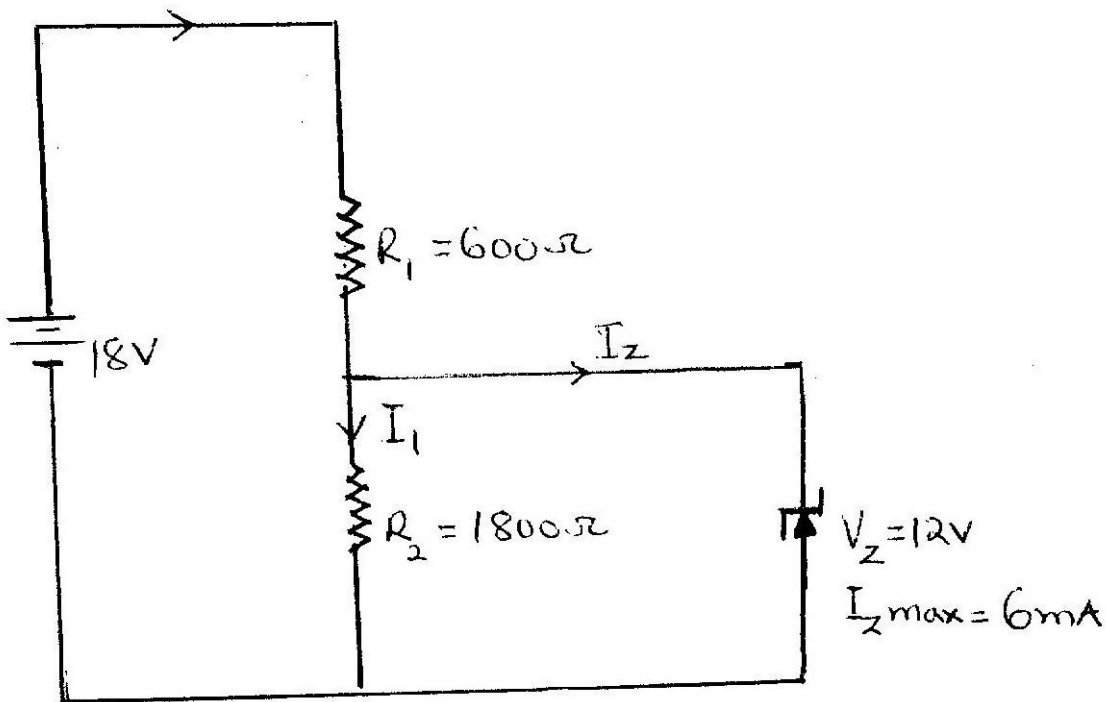


Fig. 1

- ii. Draw the symbol for a photodiode and state its uses. [3 marks]
- c). i. Define fabrication. [1 mark]
- ii. Discuss the processes of fabrication of a BJT transistor. [4 marks]

QUESTION THREE

- (a) Explain the difference between field effect transistor and bipolar junction transistor [3 marks]
- (b) The circuit below represents abias connection. Use the circuit to answer questions that follow.



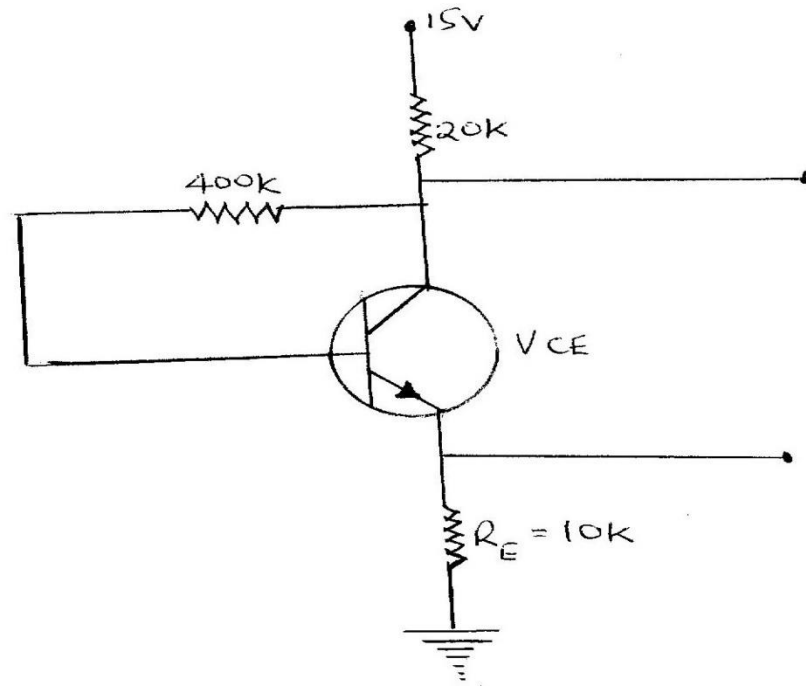


Fig.2

Find

- i). $I_{C(sat)}$ [2 marks]
- ii). V_{CE} [3 marks]
- iii). K_{β} neglect V_{BE} and take $\beta=100$ [2 marks]
- c). i. Define Quiescent point [1 mark]
- ii. For the circuit below draw the d.c load line and locate its Quiescent or dc working point. [4 marks]



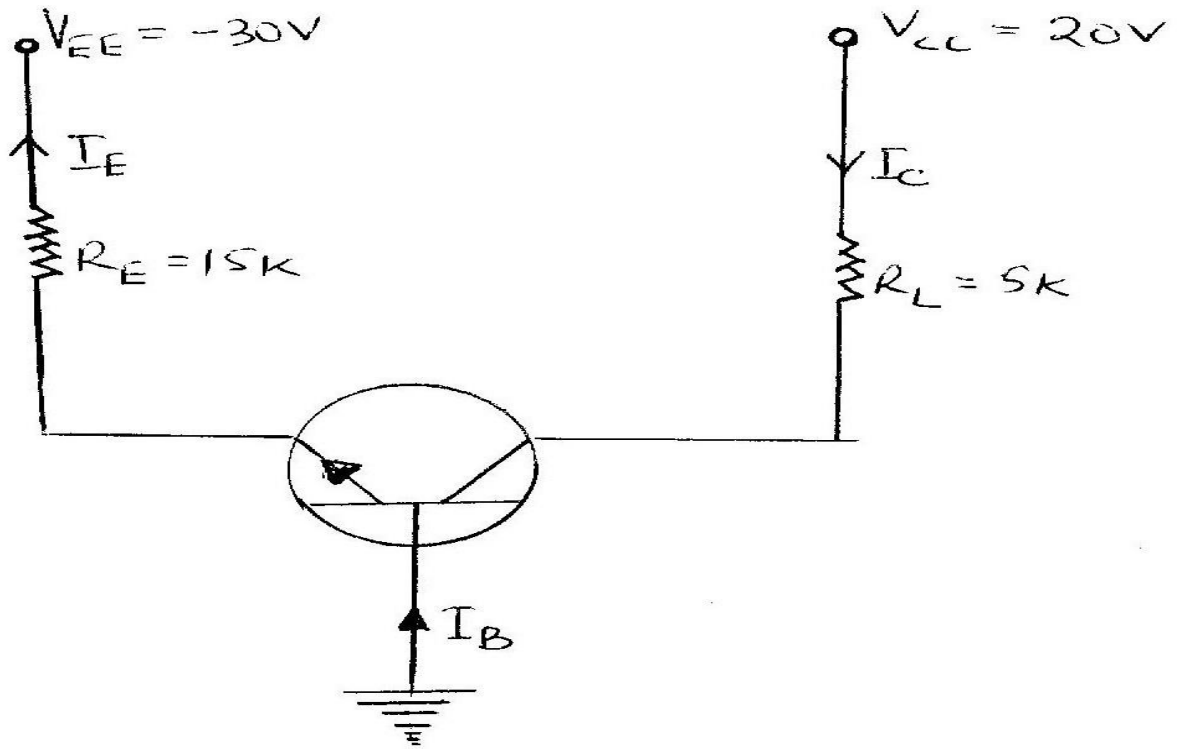


Fig. 3

QUESTION FOUR

- a). state and describe any two optoelectronic devices that are made from semiconductors p-n junction. **[5 marks]**

- b).
 - i. State the use of Thevenin's theorem in a circuit. **[1 mark]**

 - ii. Apply Thevenin's theorem to find equivalent resistance (R_{th}), current through the 3Ω resistor and Thevenin's voltage (V_{th}) **[6 marks]**



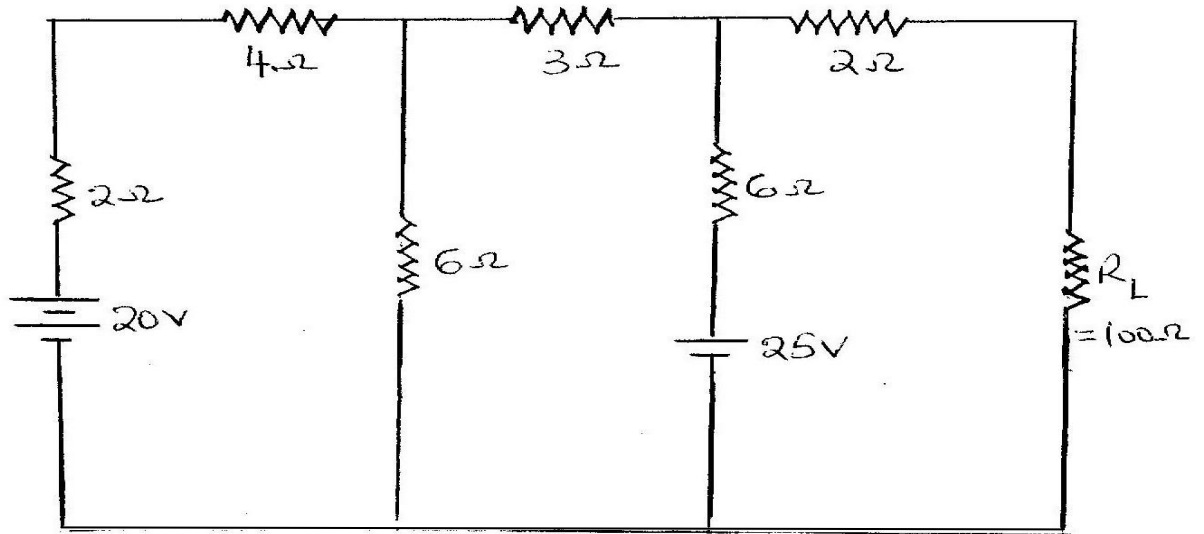


Fig. 4

- iii. State the condition and disadvantages of Mesh analysis. [3 marks]

QUESTION FIVE


- (a) Briefly describe the operations of a thyristor. [3 marks]
- (b) Name two applications of silicon controlled rectifiers (SRC) and function of DIACS [3 marks]
- (c) A given silicon UJT has an inter base resistance of 10K, $R_B = 6K$ with $I_E = 0$. Find
- i. UJT current if $V_{BB} = 20V$ and V_E is less than V_P [2 marks]
 - ii. Peak point voltages, V_P [2 marks]
- (d). i. Enumerate steps for drawing ac equivalent circuits [3 marks]
- ii. State Norton's theorem as applied in circuit analysis. [2 marks]

QUESTION SIX

- (a) i. Superposition theorem has widespread applications in electricity and electronics. State two uses of this theorem. [2 marks]



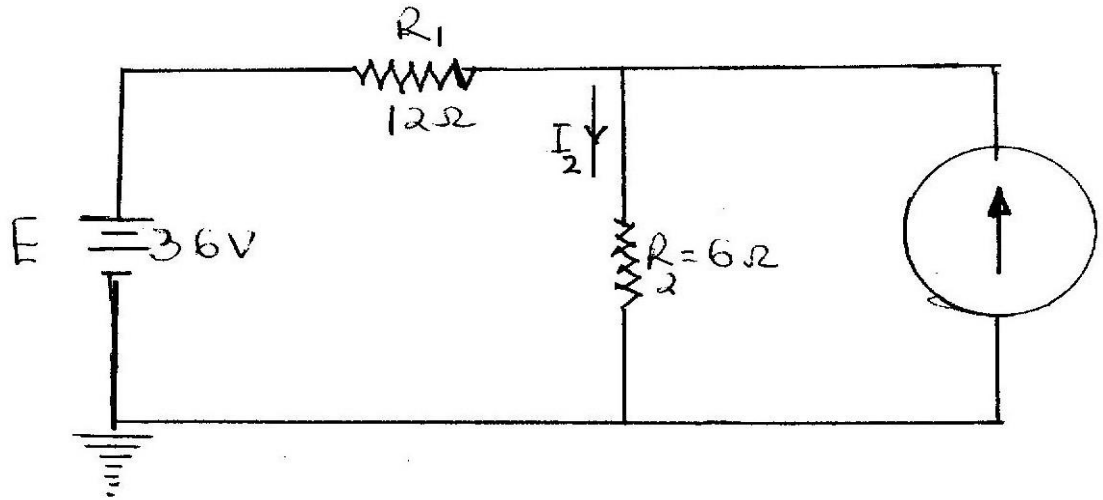- ii. Using Superposition theorem determine the current through resistor R_2 for the network in fig5 below. [4 marks]



- i. Fig .5
- ii. In the above circuit demonstrate that the Superposition theorem is not applicable to power levels [2 marks]
- (b) Describe fully the bridge full wave rectifier circuit. [4 marks]
- (c) Small signal amplifiers also referred to as voltage amplifiers have three main properties. State and define these properties. [3 marks]

